

MEMO

Drexel University

To: Dr. Christopher Peters, ECE 303 Fall 2020

From: Dinh Nguyen

Date: Oct 16st, 2020

Re: Lab 3 Pulse Width Modulation

Purpose

Photoresistor or photocell is a device that is used to detect surrounding light and change its resistor accordingly. The goal of the lab is to study the behavior of the photoresistor, how to use PWM to control duty cycle and brightness of LED and the relationship between the photoresistor and the LED.

Discussion

Hardware: Figure 1 shows how the photoresistor and the LED are connected in series with a 1k Ohm resistor to the Arduino board. Photoresistor will be connected to pin A0 to read its voltage in bits. LED will be connected to pin 5 to be controlled by PWM and duty cycle to adjust its brightness.

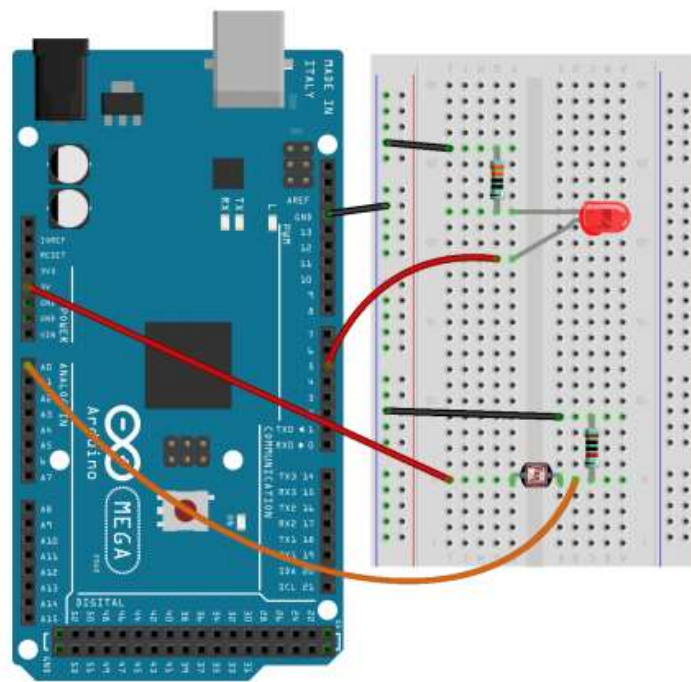


Figure 1. Photoresistor and LED circuit

Software: In order to change the duty cycle over time, a for loop is used to add up 5% at a time for duty cycle variable. It is then multiplied by the OCR of the timer to control the frequency of the input signal to the LED. Because the frequency is too fast, our human eyes can only see the light of the LED is increasing

over time. The duty cycle will be reset when reaching 100%. Using analogRead, photocell reading will be recorded in bits and from that, we can calculate the voltage across the photocell by dividing the reading by 255 bits and multiply by 5. Since the photocell is in series with the resistor, the voltage across the resistor in photocell circuit is 5 – voltage of photocell. On the other hands, the voltage across the LED is equivalent to 5 (the input voltage) multiplied by the duty cycle. Thus, the voltage across the resistor of the LED circuit is 5-voltage of LED. We will use serial terminal to output the voltages across the resistors in both circuit and the duty cycle. From the data collected, we can develop some plots to study the relationship between LED and photocell.

Plots

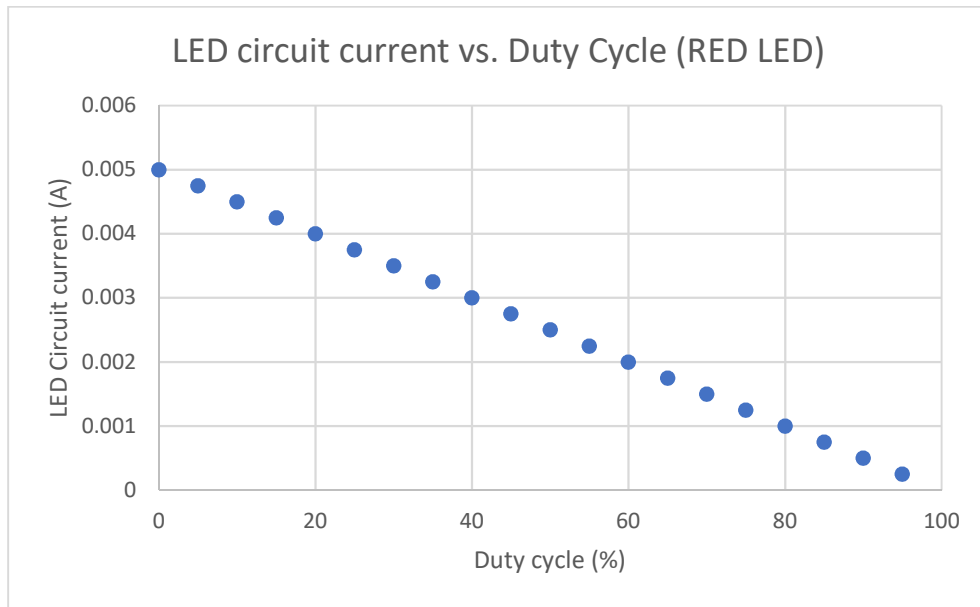


Figure 2. LED current vs Duty cycle of RED LED

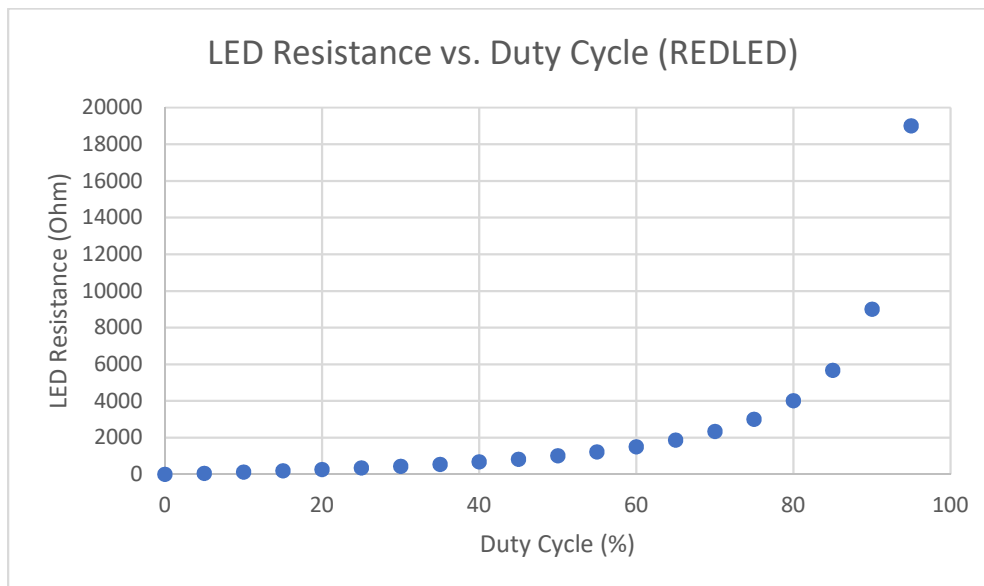


Figure 3. LED Resistance and Duty cycle of RED LED

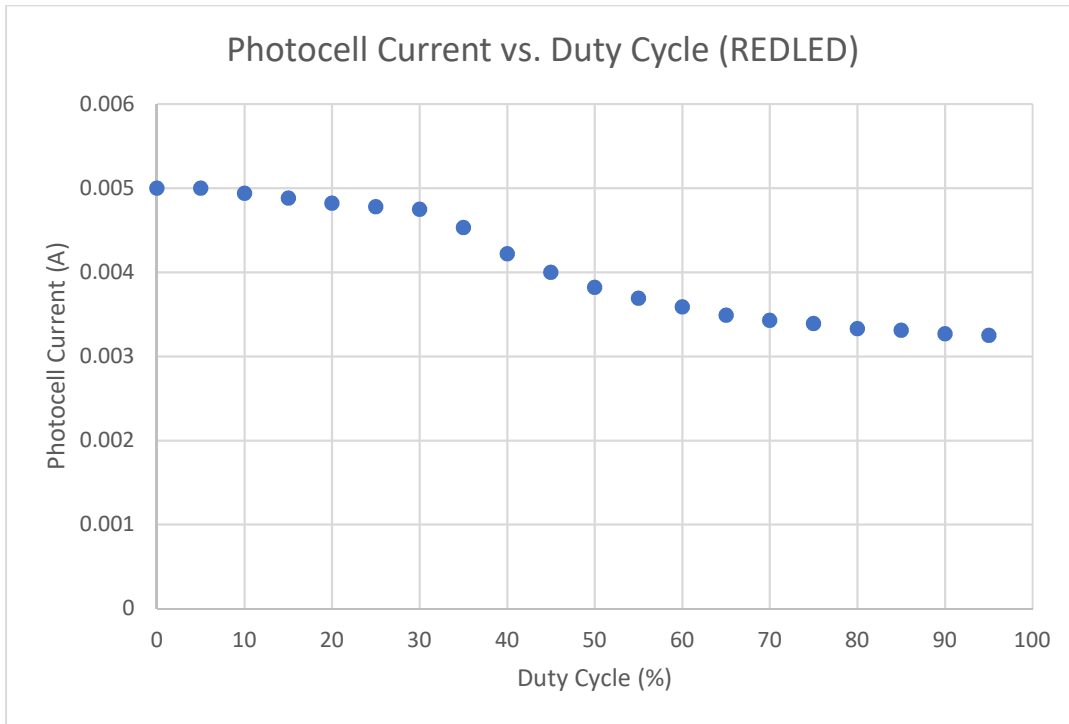


Figure 4. Photocell Current vs Duty cycle of RED LED

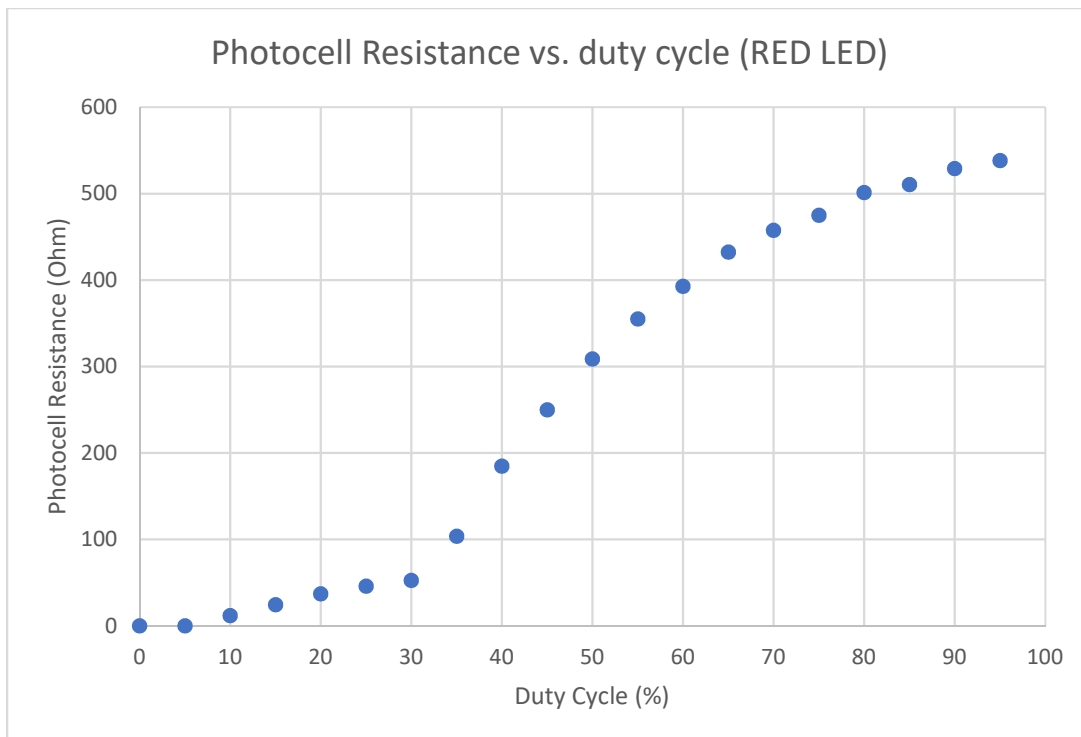


Figure 5. Photocell Resistance vs. Duty Cycle of Red Led

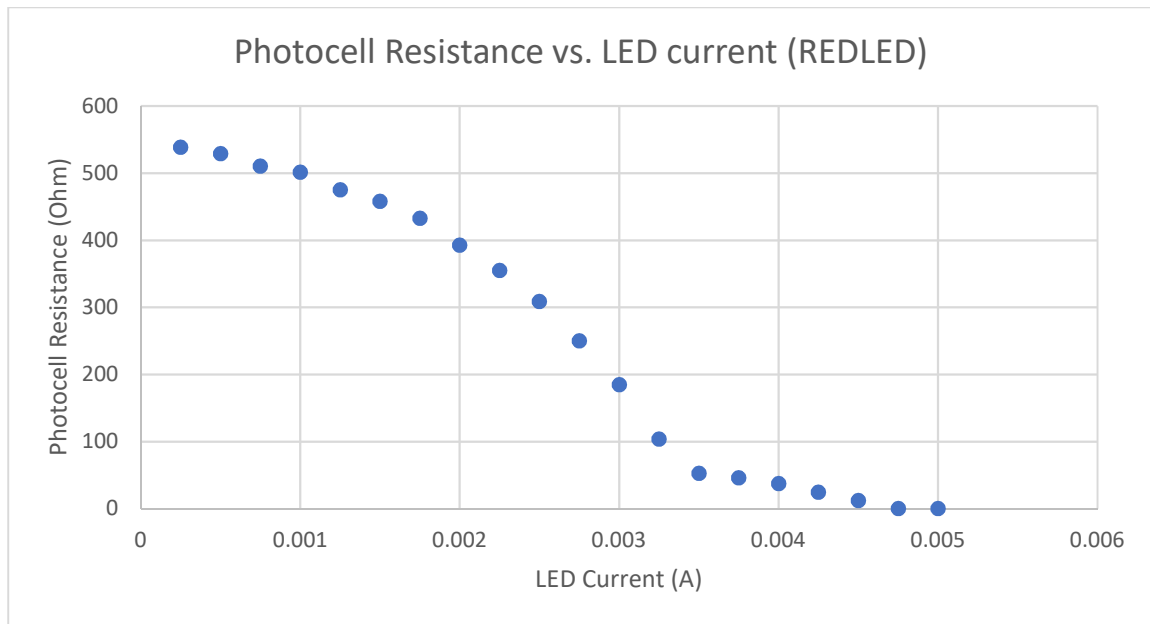


Figure 6. Photocell Resistance and LED current of RED LED

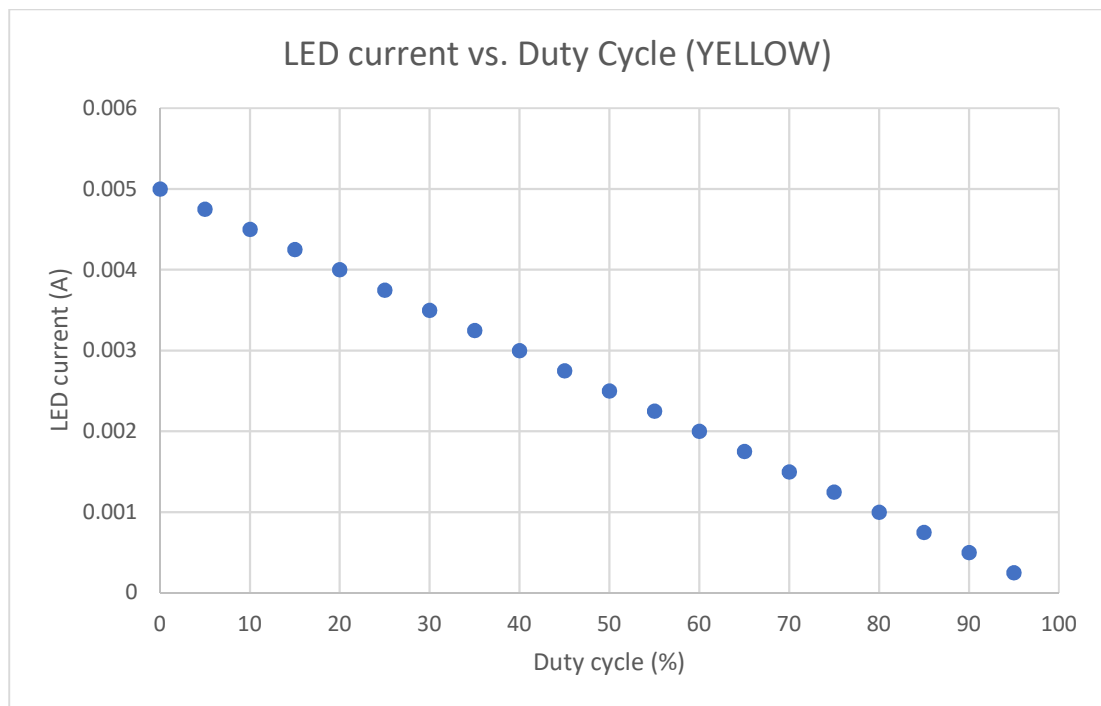


Figure 7. LED current vs Duty cycle of Yellow LED

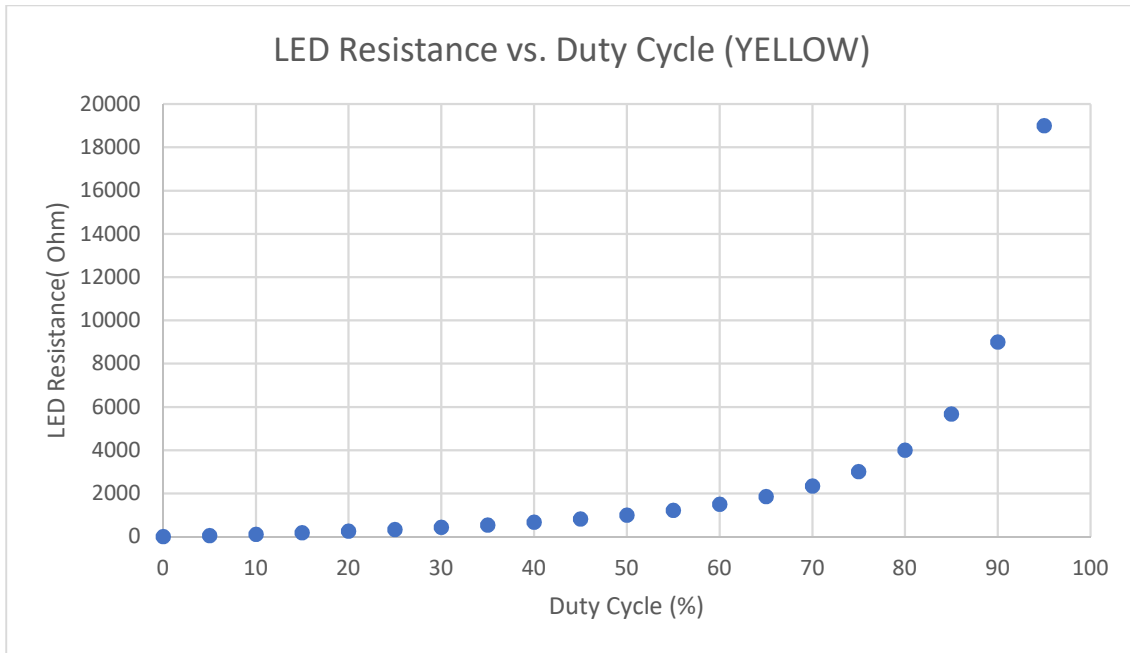


Figure 8. LED Resistance vs Duty Cycle of Yellow LED

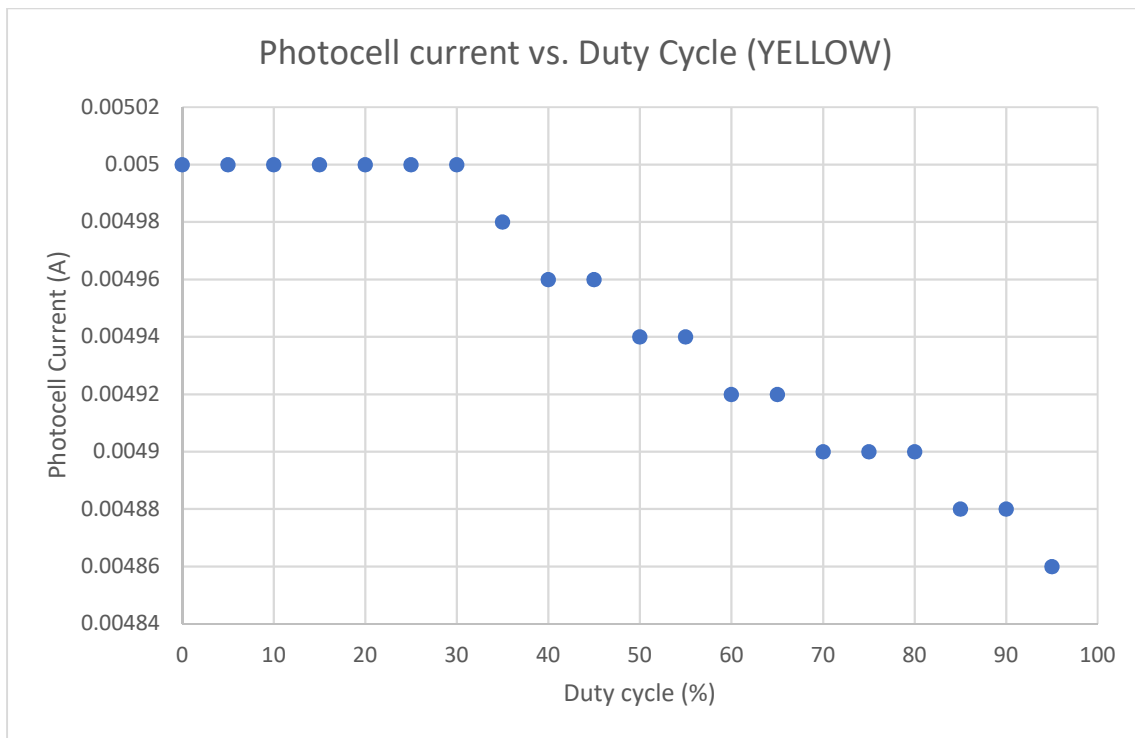


Figure 9. Photocell current and Duty cycle of Yellow LED

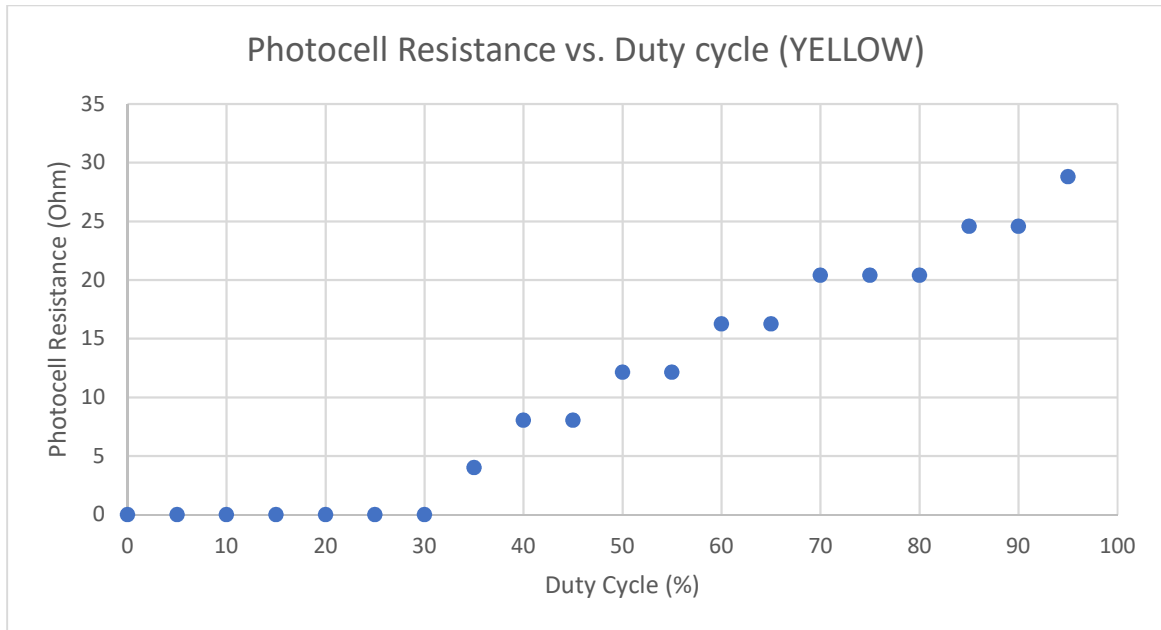


Figure 10. Photocell Resistance and Duty Cycle of Yellow LED

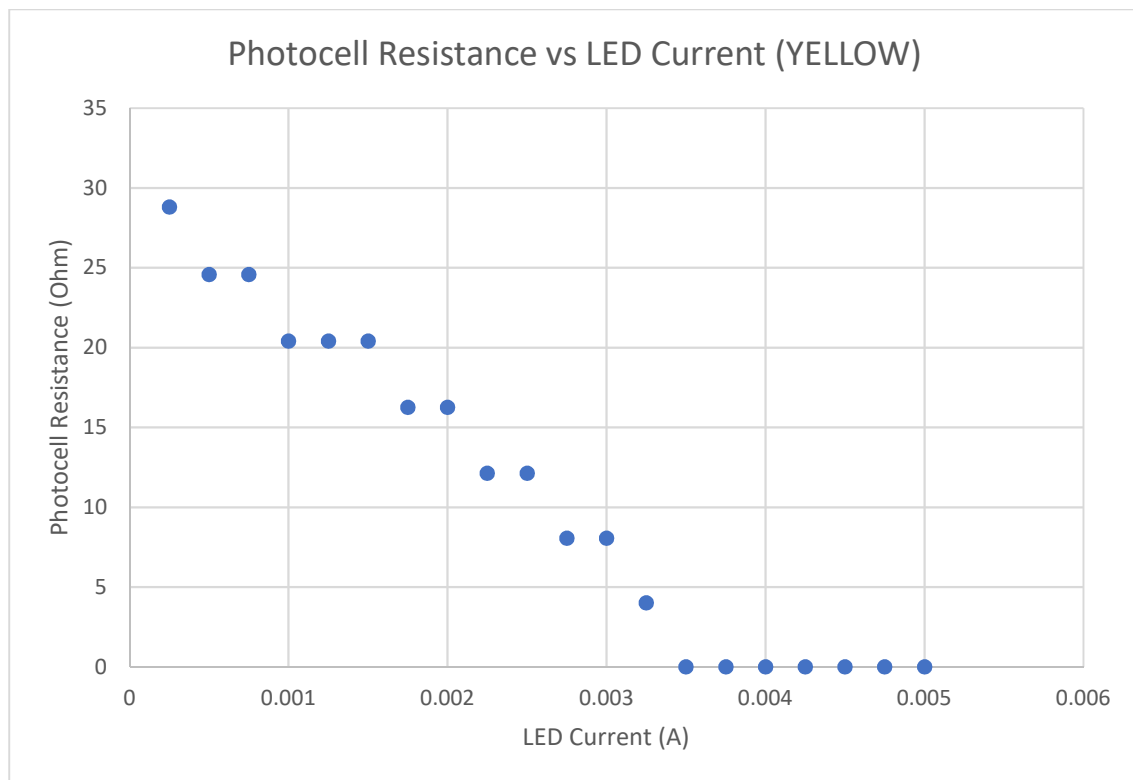


Figure 11. Photocell Resistance vs LED current of Yellow LED

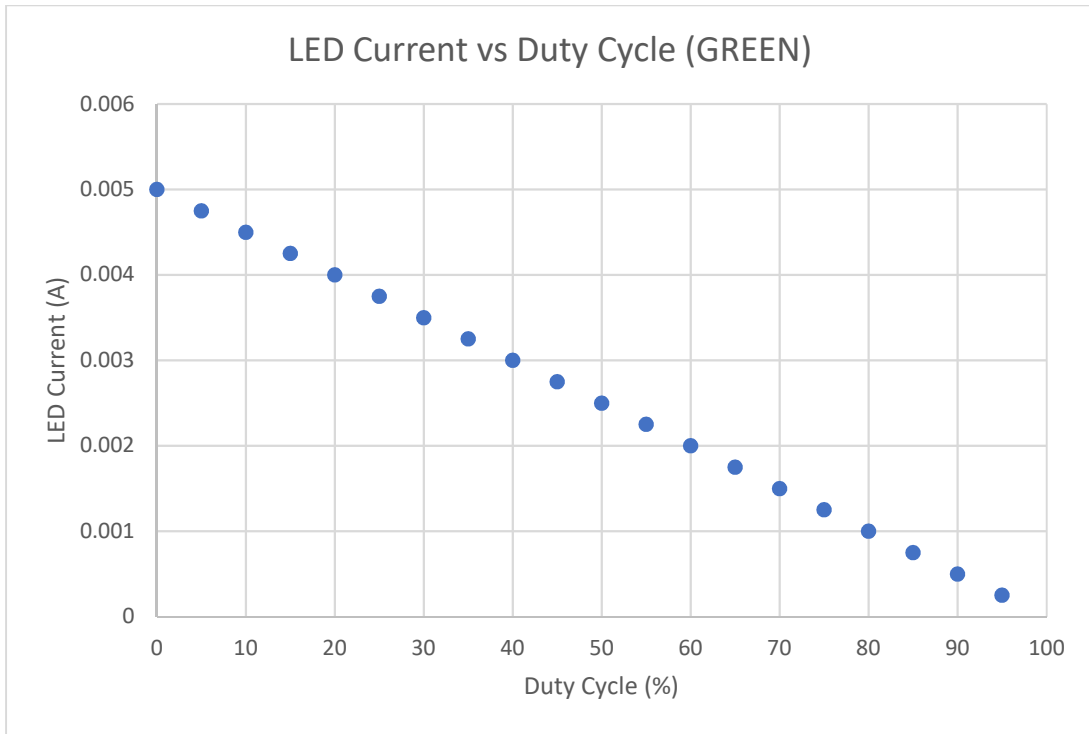


Figure 12. LED Current vs Duty Cycle of Green LED

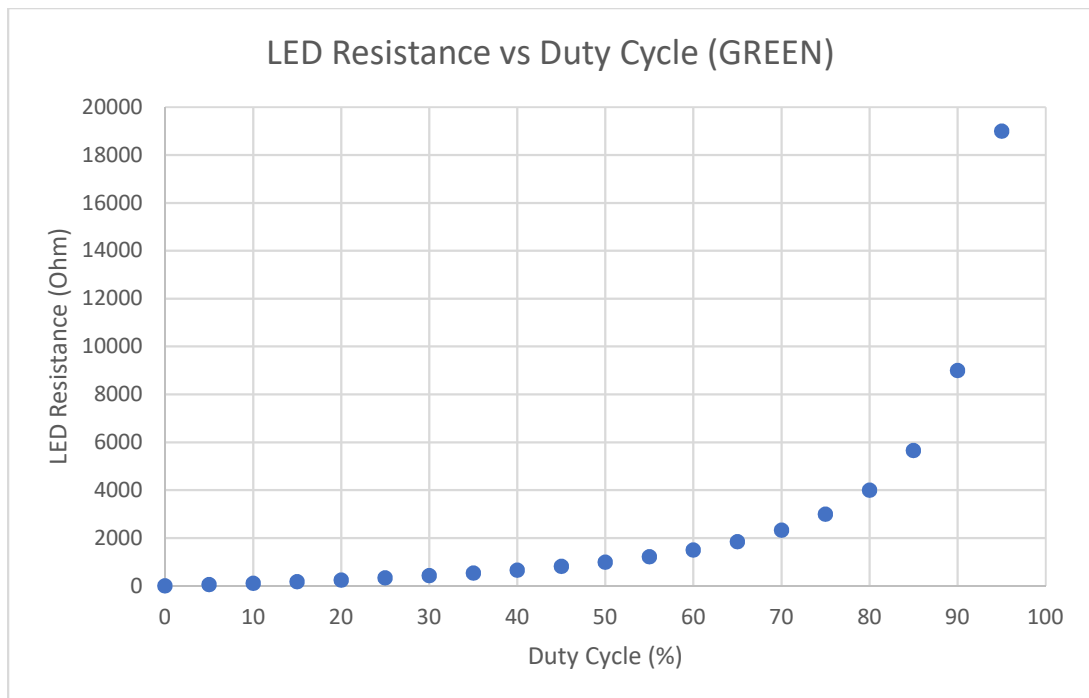


Figure 13. LED Resistance vs Duty Cycle of Green LED

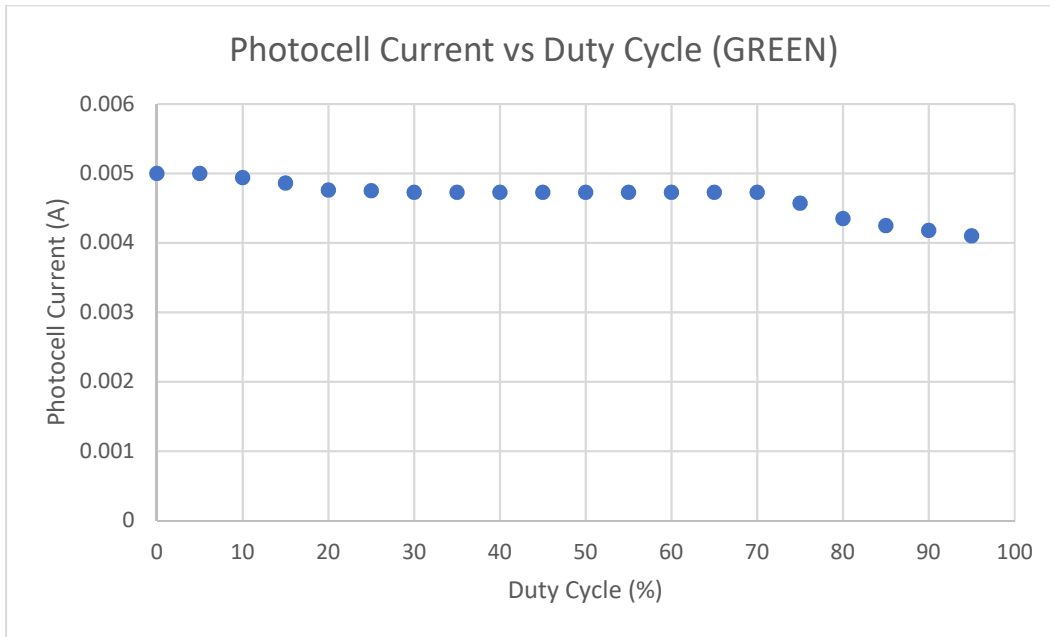


Figure 14. Photocell Current vs Duty cycle of Green LED

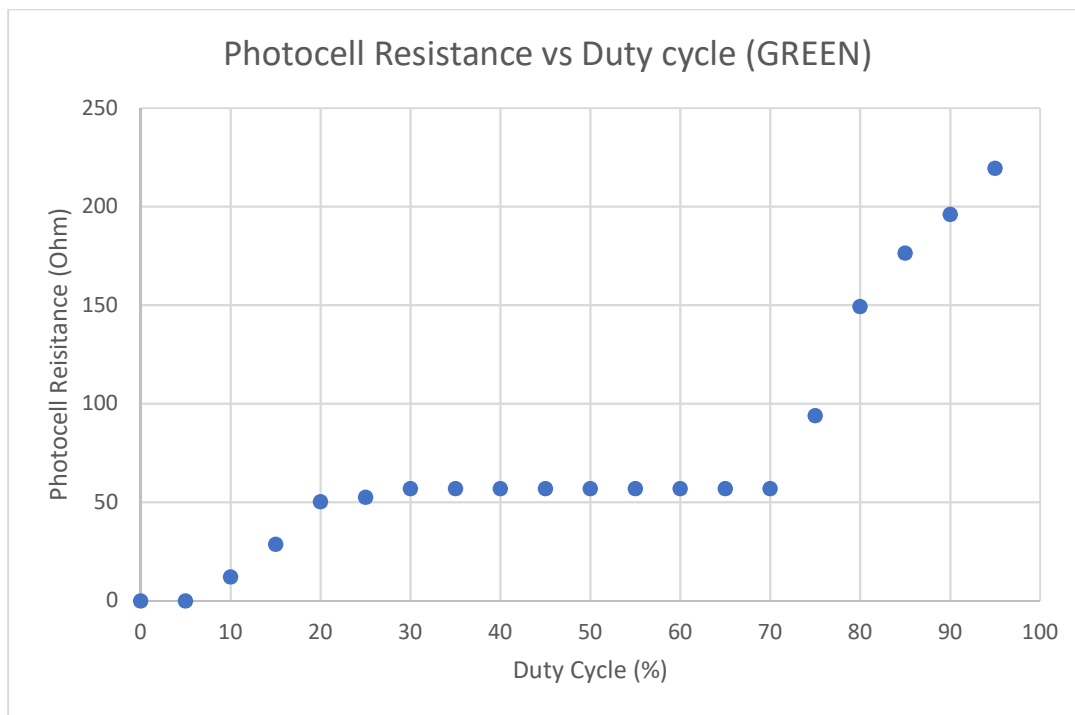


Figure 15. Photocell Resistance vs Duty Cycle of Green LED

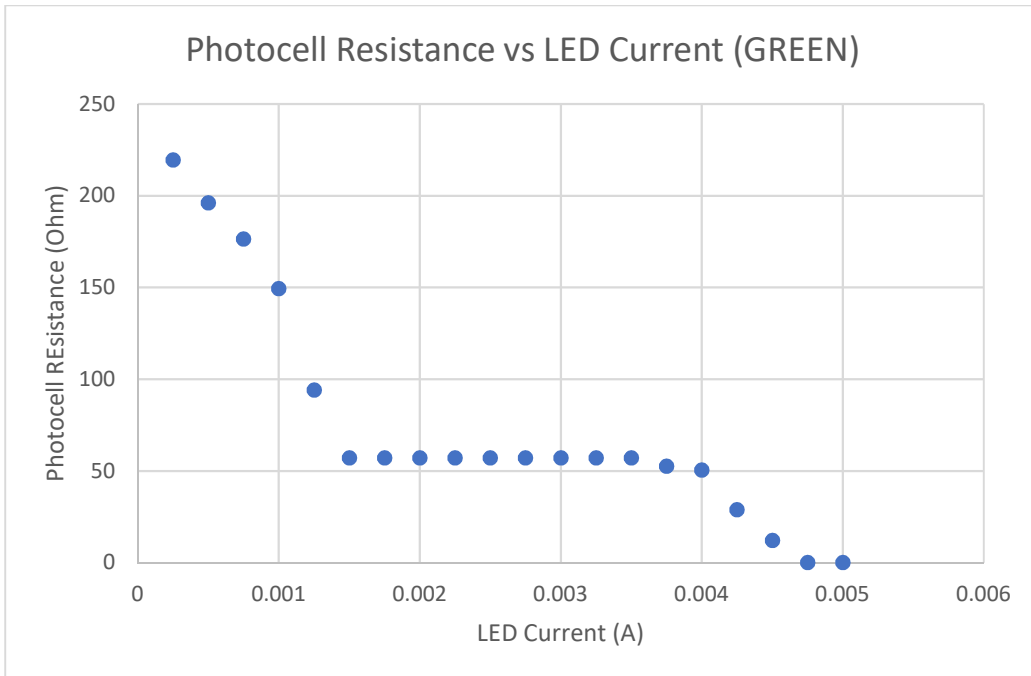


Figure 16. Photocell Resistance vs LED Current of Green LED

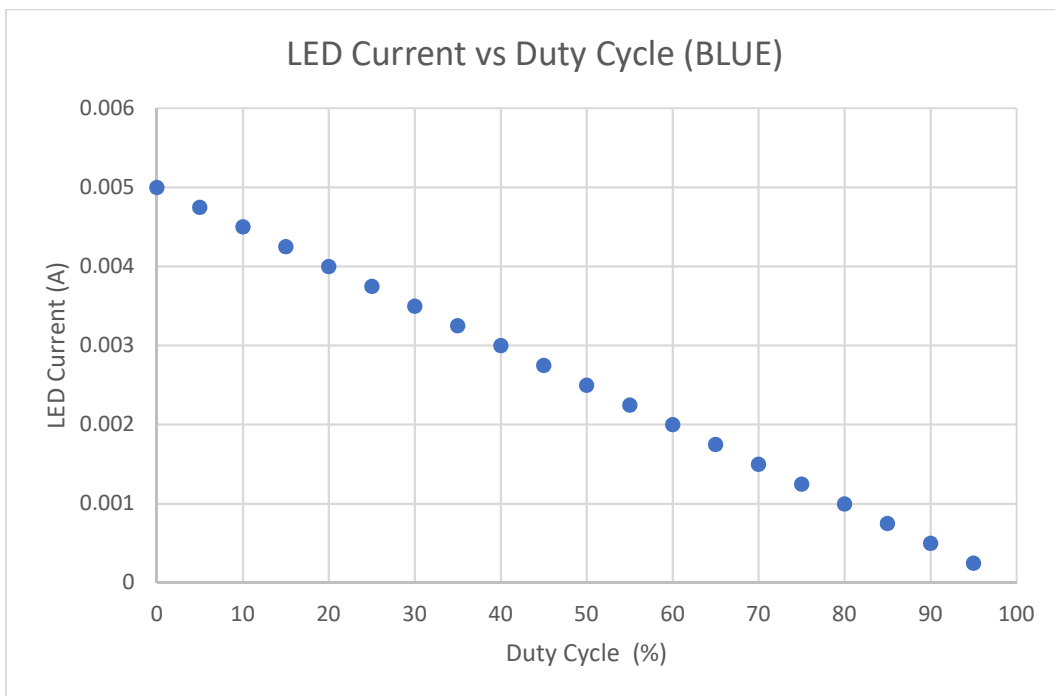


Figure 17. LED Current vs Duty Cycle of Blue LED

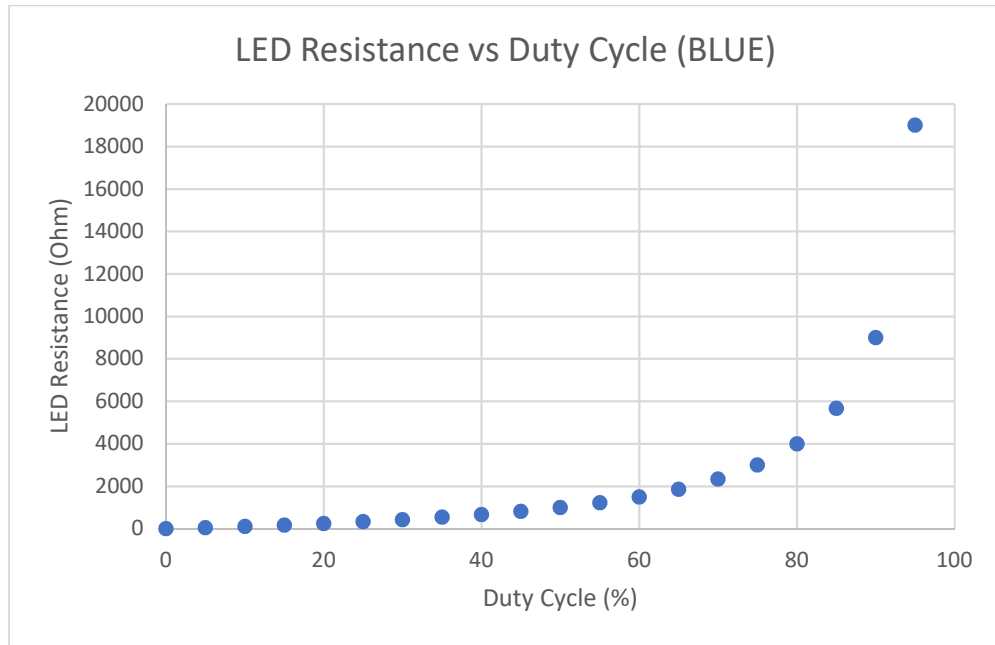


Figure 18. LED Resistance vs Duty Cycle of Blue LED

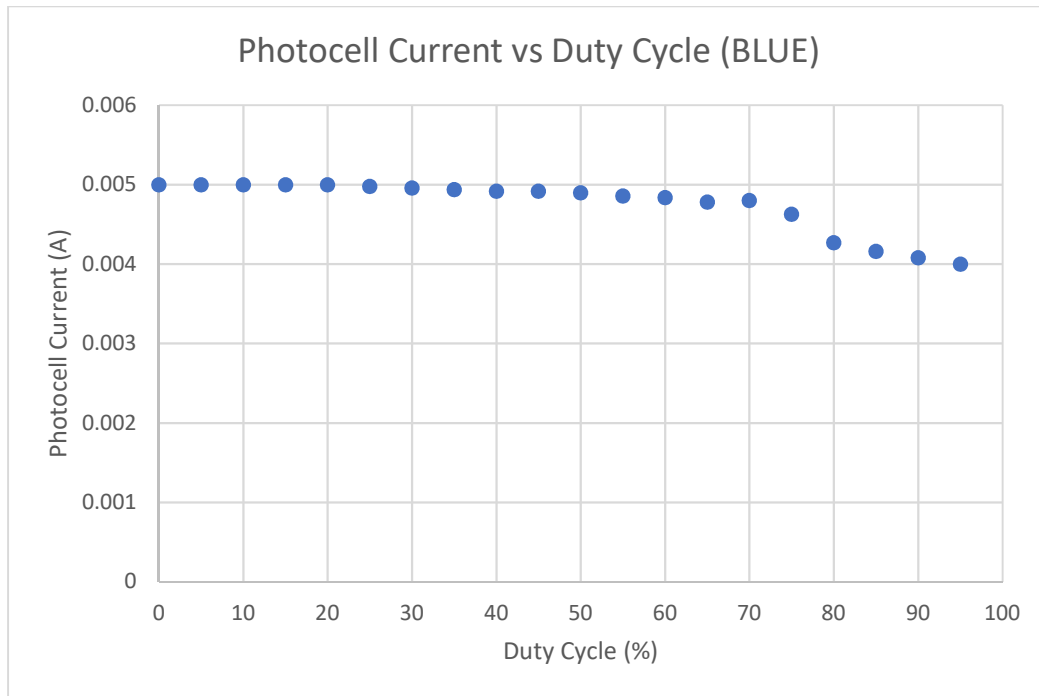


Figure 19. Photocell Current vs Duty Cycle of Blue LED

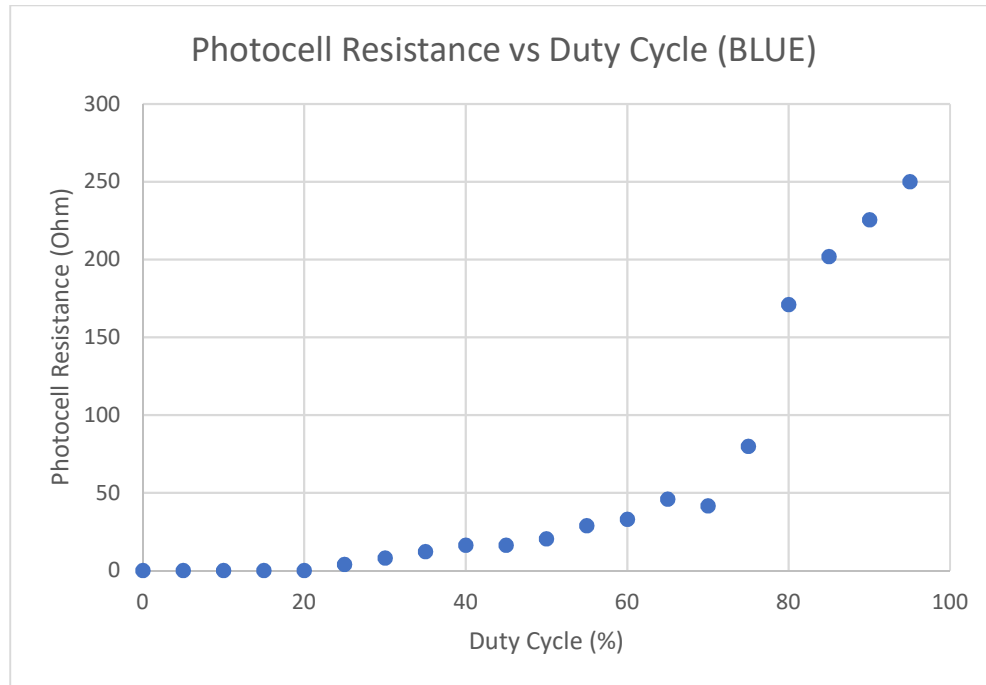


Figure 20. Photocell Resistance vs Duty cycle of Blue LED

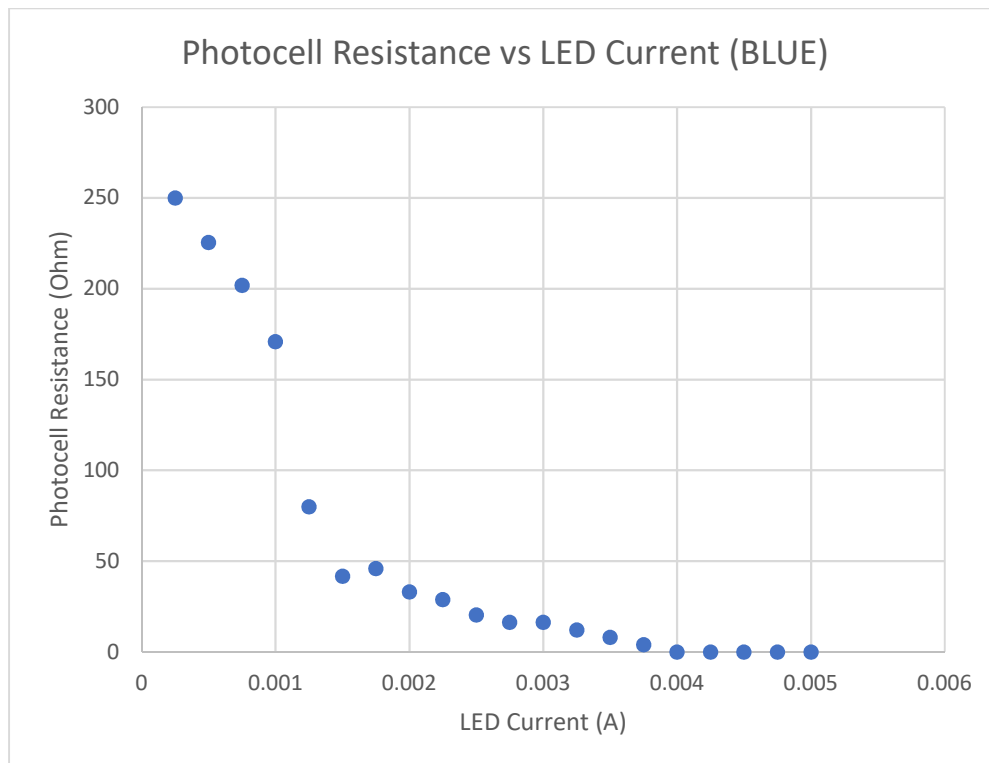


Figure 21. Photocell Resistance vs LED Current of Blue LED

Recommendation

From the plots, we can observe a variation in the data points which is due to the inconsistency of the testing environment and the performance of the photocell. A slight spot of light can easily alter the data and distort our graph. Additionally, the distance between the LED and the photocell also affects the results and it is difficult to keep the distance the same when switching between different LEDs. Those limitations will be responsible for the variety of the data collected. However, we can see an overall pattern among the 4 LEDs. The LED current always goes down as the duty cycle goes up, this is because the voltage across the LED increases, the voltage across the resistor will decrease while the resistor value remains unchanged. The same scenario will happen for the photocell circuit, however the data is more distorted and we can only observe a slight decrease in the current. Moreover, the Red LED seems to produce a more significant contact with the photocell compared to the other LEDs. Further experiments with better testing environment and more detailed data points (1% duty cycle margin for example) need to be carried out to improve the results and analysis.

Arduino Sketch

```
lab3

int ledpin = 5;
float templ=0;
float dutycycle = 0.05;
int photocellPin = 0;      // cell at a0
int photocellReading;
int count = 0;
float volLED = 0.0;
float volphoto = 0.0;

void setup() {
  // Timer 3 - Fast PWM
  TCCR3A=0b10000010;
  TCCR3B=0b00011100;
  OCR3A= 1000;
  ICR3 = 1000;
  TCNT3=0;
  pinMode(ledpin,OUTPUT);
  Serial.begin(9600);
  interrupts();
}

void loop() {
  //count += 1;
  for (dutycycle = 0; dutycycle <= 1.0; dutycycle +=0.05){
    templ = dutycycle*ICR3;
    OCR3A = (int) templ;
    delay(2000);
    photocellReading = analogRead(photocellPin);
    Serial.print("duty cycle = "); Serial.println(dutycycle);
    Serial.print("photoread = ");Serial.println(photocellReading);
    volLED = 5 - dutycycle*5;
    Serial.print("voltage resistor LED circuit = "); Serial.println(volLED);
    volphoto = 5 - photocellReading*5.0/255.0;
    Serial.print("voltage resistor photocell circuit= "); Serial.println(volphoto);
  }
  // for (dutycycle = 1.0; dutycycle >= 0.05; dutycycle -=0.05){
  //   templ = dutycycle*ICR3;
  //   OCR3A = (int) templ;
  //   delay(2000);
  //   photocellReading = analogRead(photocellPin);
  //   Serial.print("photocell reading = ");
  //   Serial.println(photocellReading);      // raw analog reading
  // }

}

ISR(TIMER3_COMPA_vect){
  digitalWrite(ledpin, !digitalRead(ledpin));
}
```